



[Home](#) | [XBOX](#) | [XERC](#) | [Led Fader](#) | [Forums](#) | [Contact](#)

[XERC 2](#) | [XERC CME SE](#)

XERC 2

[Home](#)

[About](#)

[Build It](#)

[Overview](#)

[Hardware](#)

[Firmware](#)

[Programming](#)

[Install It](#)

[Support](#)

[Buy It!](#)

Hardware of the XERC 2


The XERC 2 is built around the attiny45 mcu. It is a pin compatible upgrade from their attiny15 mcu. But the pin compatibility is pretty much everything they have in common, the new attiny15/45/85 series a much better architecture and can thus perform more complex tasks. This is the brains of the XERC 2, it receives and decodes the signal from the IR-module and controls all output signals.

Pablot's XBOX360 fund

Feel free to donate if you found this site usefull. All money will go towards buying a new XBOX360 for future tutorials and small hardware addition.



Schematic and parts:

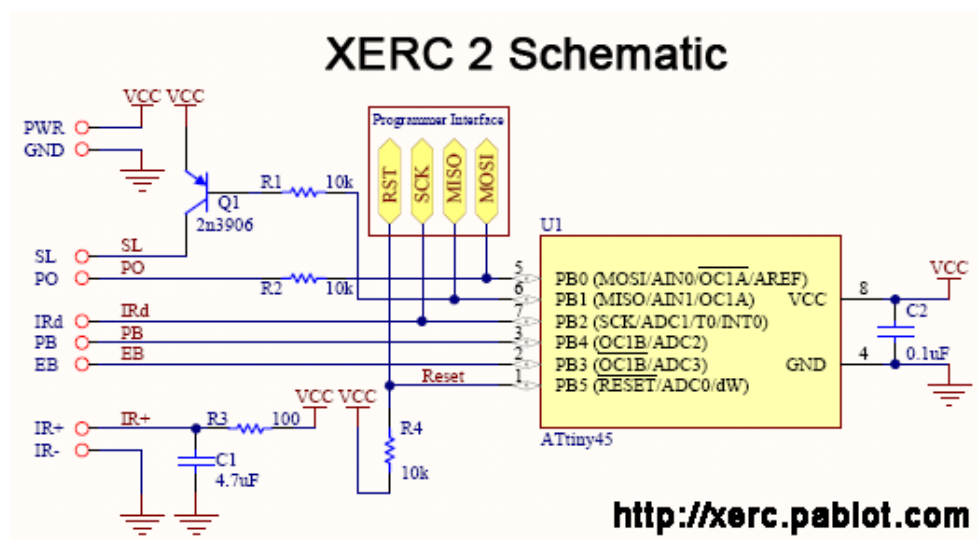

And here is the part list.

Part ID	Description	Comment
C1	4.7uF electrolytic capacitor	-
C2	0.1uF Ceramic Capacitor	-
R1,R2,R4	10kOhms resistors	-
R3	100ohms resistor	-
Q1	2n3906 PNP transistor	-
U1	ATtiny45	-
-	TSOP32156 IR-module	2.7-5.5V supply voltage.
-	8-pin dip socket	Socket if you want to be able to remove the ATtiny45.
-	LED	If you don't want to use the eject led in the xbox.

ATtiny15/25/45/85 ISP programmer connection:

This is how the ISP programming header is connected to the attinyx5 series.

Top View

